

# Asynchronous Logic II

# Hazards


- In designing asynchronous sequential circuits, care must be taken to conform with certain restrictions and precautions to ensure that the circuits operate properly. The circuit must be operated in **fundamental mode** with only one input changing at any time and must be **free of critical races**.
- There is another phenomenon, called a **hazard**, that may cause the circuit to malfunction.
- Hazards are **unwanted switching transients** that may appear at the output of a circuit because different paths exhibit different propagation delays.

# Hazards in Combinational Circuits


- Hazards occur in combinational logic, which may cause a temporary false output value.
- **Static hazard** is a momentary change in the output value when no change should occur.
- static-1 hazard: logic 1 momentarily goes to 0.
- static-0 hazard: logic 0 momentarily goes to 1.
- **Dynamic hazard**: logic level goes through three or more transitions.



(a) Static 1-hazard

 


(b) Static 0-hazard

 

(c) Dynamic hazard


# Static-1 Hazards

 

- Two parallel paths connected to an OR gate
- One path with an inverter.
- If  $x$  changes, different delays on two paths cause logic 1 momentarily goes to 0

 
# Static-1 Hazards

- The **sum-of-products** (AND-OR circuit) may have a **static-1** hazard.
- Initially  $x_1x_2x_3 = 111$ ,  
the output of the 1st gate is 1  
the output of the 2nd gate is 0  
the output of the 3rd gate is 1
- Then the input  $x_2$  makes the transition from 1 to 0.




 
# Static-1 Hazards

- Gate 1 output makes the transition  $1 \rightarrow 0$
- Gate 2 output makes the transition  $0 \rightarrow 1$
- Gate 2 does not respond as quickly because of the propagation delay through the inverter.
- As result there is a moment when both inputs to gate 3 are 0 and so the output will transition to 0 and then return to 1.


  
# Static-1 Hazards


- The Karnaugh Map can be used to identify and remove hazards.
- In this circuit the transition of  $x_2$  from 1 to 0 corresponds to the transition between the minterms 111 and 101



$$Y = x_1x_2 + x'_2x_3$$
 
# Static-1 Hazards

- If another gate is added to the circuit corresponding to the product term  $x_1x_3$ , the hazard is removed.
- This because the output of the new gate will keep the output at logic 1 despite the momentary transition.
- In general hazards can be removed by covering hazard minterms with a common product term.




$x_2x_3$

	00	01	11	10
$x_1$				
0		1		
1		1	1	1

$$Y = x_1x_2 + x'_2x_3 + x_1x_3$$



# Static-0 Hazards

 


- Two parallel paths connected to an AND gate
- One path with an inverter.
- If x changes, different delays on two paths cause logic 0 momentarily goes to 1

# Static-0 Hazards

- If circuit in **product-of-sums** form:

$$Y = (x_1 + x_2')(x_2 + x_3)$$

Cause **static-0** hazard.

 

- Add extra redundant terms to fill the gap:

$$Y = (x_1 + x_2')(x_2 + x_3)(x_1 + x_3)$$

*Hazard*


		$x_2x_3$			
$x_1$		00	01	11	10
0	0			0	0
1	0				

$$Y = (x_1 + x_2')(x_2 + x_3)(x_1 + x_3)$$


Add another term to remove hazard
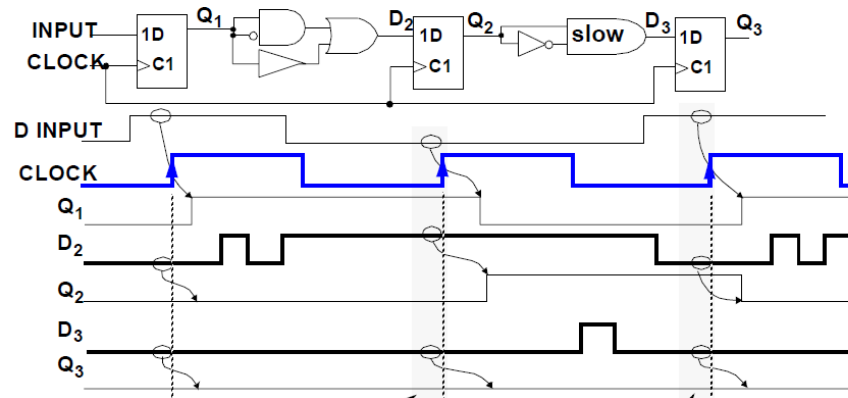
# Hazards in Sequential Circuits

- In normal combinational-circuit design associated with **synchronous** sequential circuits, hazards are of **no concern**, since momentary erroneous signals are not generally troublesome.



 - However, if a momentary incorrect signal is **fed back** in an asynchronous sequential circuit, it may cause the circuit to go to the **wrong stable state**.



(a) Logic diagram

	$x_1x_2$			
	00	01	11	10
$y$				
0	0	0	1	0
1	1	0	1	1

(b) Transition table

	$x_1x_2$			
	00	01	11	10
$y$				
0			1	
1	1		1	1


(c) Map for Y

**Need to add an extra gate**  
 $Y = x_1x_2 + x_2'y + x_1y$

- If the circuit is in total stable state  $yx_1x_2 = 111$  and input  $x_2$  changes from 1 to 0, the next total stable state should be 110.
- However, because of the hazard, output Y may go to 0 momentarily. If this false signal feeds back into gate 2 before the output of the inverter goes to 1, the output of gate 2 will remain at 0 and the circuit switch to the incorrect total stable state 010.

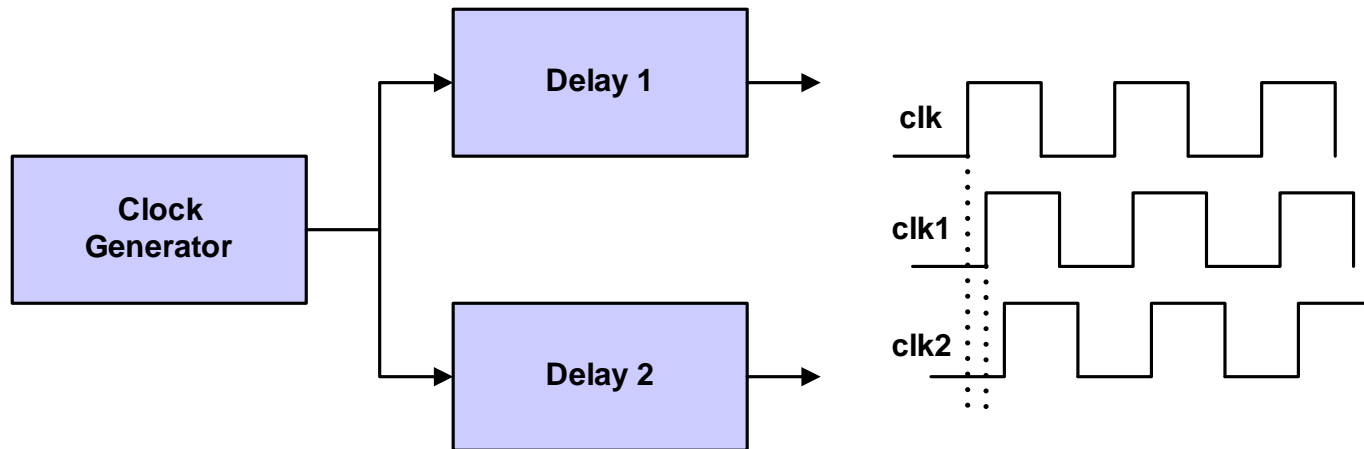
# Clock Skew

- A single clock generator is producing a waveform for distribution to two parts of a digital system
  - Both clock waveforms should be occurring at the same time however due to the different logic paths, one clock lags behind the other.
  - The time delay between the two clock pulses is called **clock skew**.


 
# Clock Skew

- Clock skew is not a problem at low frequencies, but at high frequencies it becomes a major problem.
- At 100MHz positive clock pulse occurs every 10 nanoseconds.
- If the clock skew is 5 nanoseconds, clock 1 and clock 2 are completely out of phase and the circuit becomes inoperative.



# Clock Skew

- In very fast systems, the length of the conductors carrying clock signals must be considered.
- In such cases the sub-units may operate best asynchronously with respect to one another.

## ***For example:***

- Consider the transmission of data between one digital system and another.
- Distance may be too great to send data in parallel format along with a clock signal.
- In such cases, the data transmission must be done asynchronously.

# Summary

- Asynchronous Logic circuits do not rely on synchronising clock signals and so are difficult to design.
- Fundamental mode ensures stability.
- Race Conditions may be non-critical or critical. Critical race conditions must be avoided.
- Static Hazards may be removed by introducing redundant logic corresponding to additional Karnaugh Map minterms/maxterms.