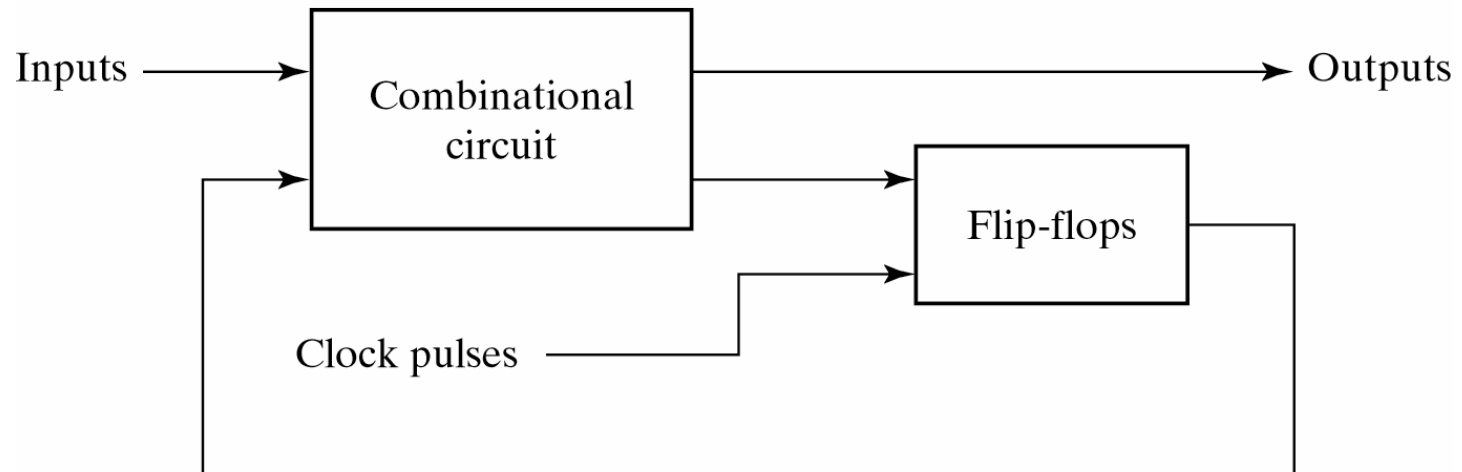


Sequential Logic II

Sequential Circuit Analysis

Sequential Logic

- Sequential logic contains both combinational logic circuits and memory storage elements (flip-flops).
- The value of the outputs of those systems is determined by external inputs and the present state of the storage elements.



Sequential Circuit Analysis

- The behavior of a clocked sequential circuit is determined from the **inputs**, the **outputs** and the **state** of its flip-flops.
- The outputs and the next state are both a function of the inputs and the present state.
- The analysis of a sequential circuit consists of obtaining a function, a table or a diagram for the time sequence of inputs, outputs and internal states.
- There are three algebraic means for describing the behavior of sequential circuits: **State Equations**, **State Table** and **State Diagram**.


Sequential Circuit Analysis

- **State Equations**
 - Specify the next state as a function of the present state and inputs

$$A(t+1) = Ax + Bx$$

$$B(t+1) = A'x$$

$$y = (A+B)x'$$

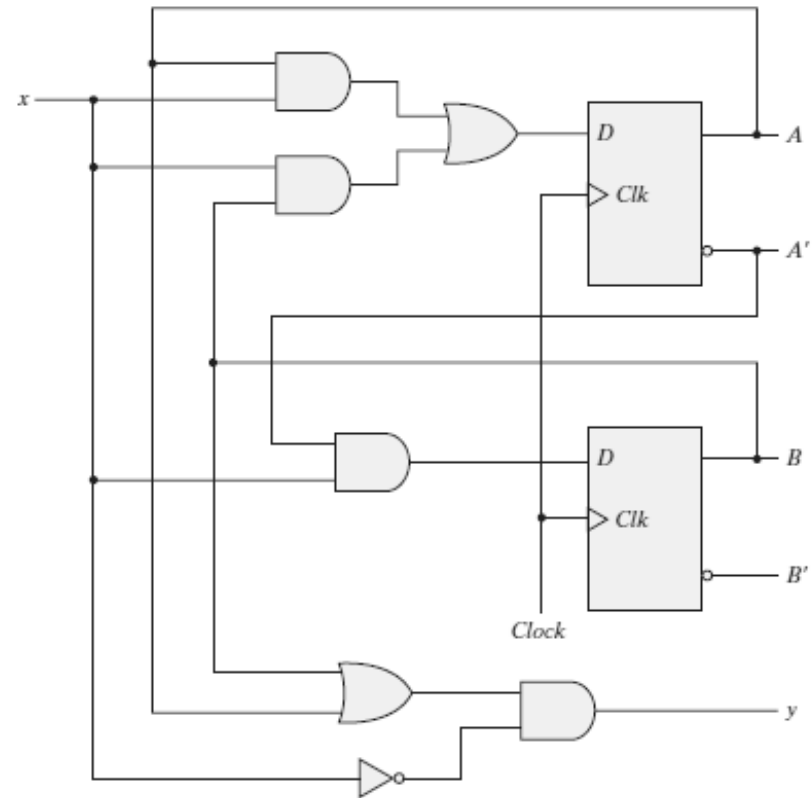


Sequential Circuit Analysis

• State Table

- The time sequence of inputs, outputs and flip-flop states can be enumerated in a state table (sometimes called a transition table).

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

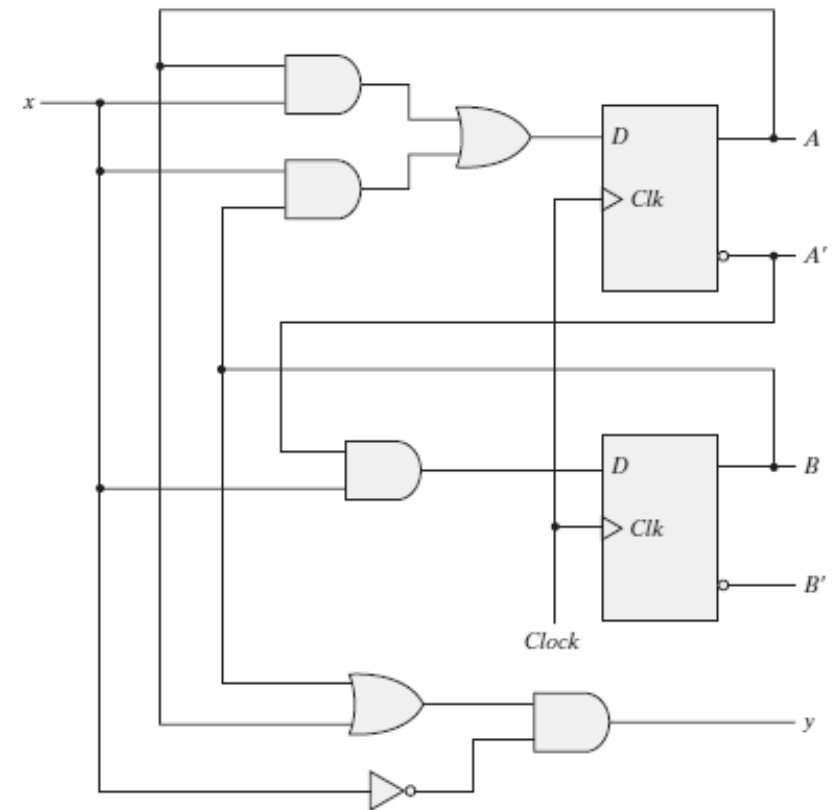


Sequential Circuit Analysis

• State Diagram

- The information available in a state table can be represented graphically in the form of a state diagram.

Second Form of the State Table


Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

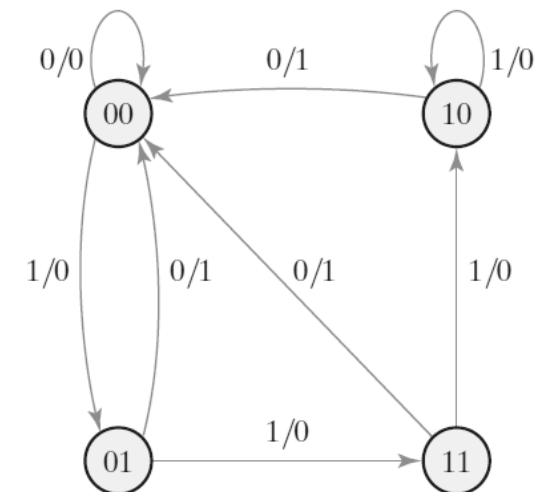


Sequential Circuit Analysis

- **State Diagram**

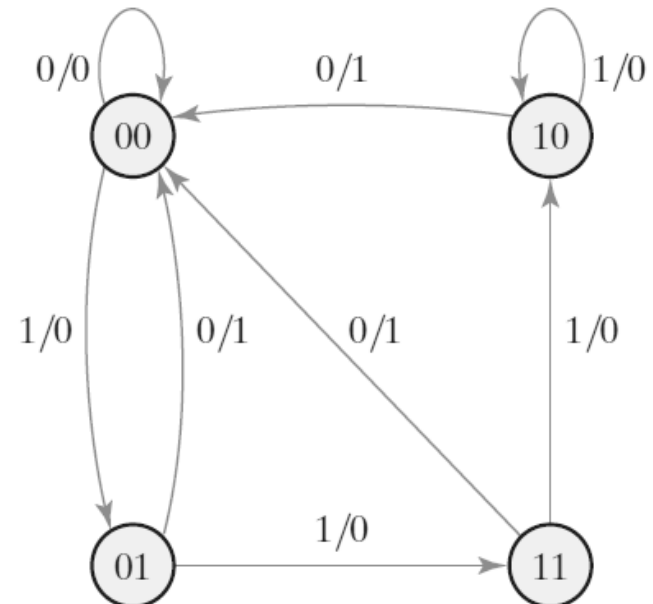- A state is represented by a circle, and the (clock-triggered) transitions between states are indicated by directed lines;
- The binary number inside each circle identifies the state of the flop-flops;
- The directed lines are labelled with two binary numbers separated by a slash (input/output).




An example sequential circuit

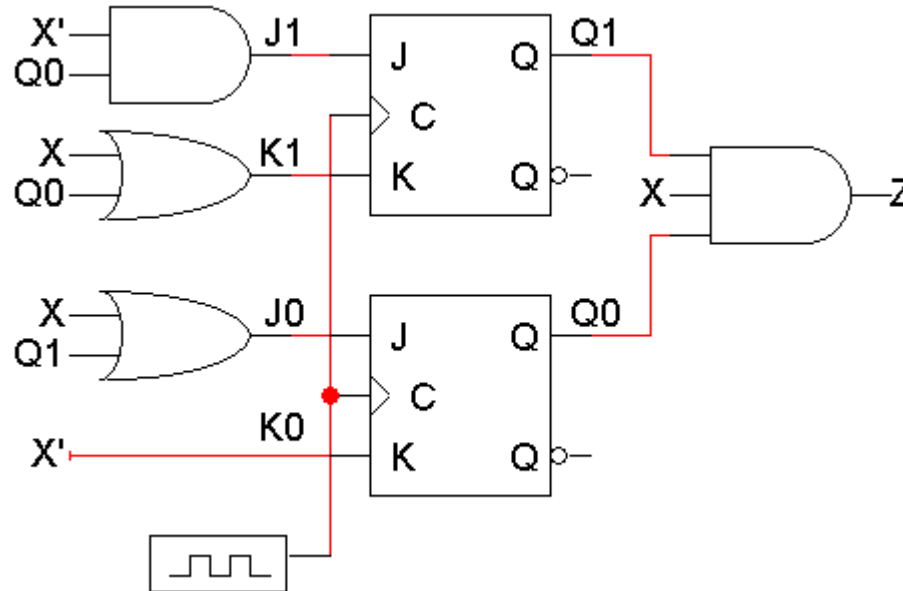

- Here is a sequential circuit with two JK flip-flops. There is one input, X , and one output, Z .
- The values of the flip-flops (Q_1Q_0) form the **state**, or the memory, of the circuit.
- The flip-flop outputs also go back into the primitive gates on the left.

Analyzing the example circuit

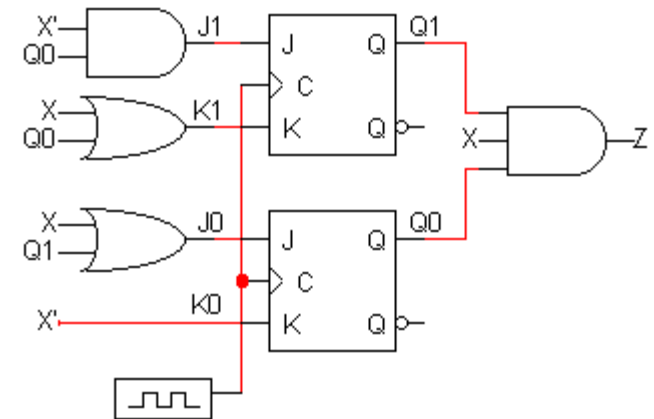- A basic state table for our example circuit is shown below.
- Remember that there is one input X , one output Z , and two flip-flops Q_1Q_0 .
- The present state Q_1Q_0 and the input will determine the next state and the output.




Present State		Inputs	Next State		Outputs
Q_1	Q_0	X	Q_1	Q_0	Z
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

The outputs are easy

- The output depends on the current state - Q_0 and Q_1 - as well as the inputs.
- From the diagram, you can see that
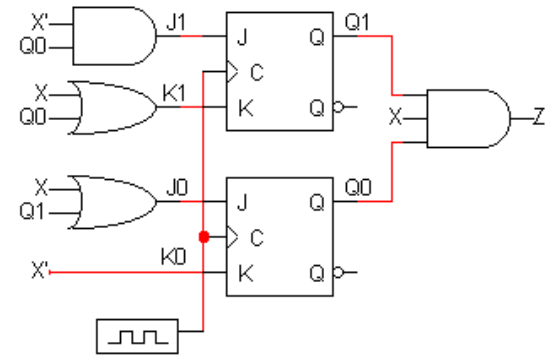
$$Z = Q_1 Q_0 X \quad \text{Output at the current time}$$



Present State		Inputs	Next State		Outputs
Q_1	Q_0	X	Q_1	Q_0	Z
0	0	0			0
0	0	1			0
0	1	0			0
0	1	1			0
1	0	0			0
1	0	1			0
1	1	0			0
1	1	1			1

Flip-flop input equations

- Finding the next states is harder. To do this, we have to figure out how the flip-flops are changing.

Step 1:

Find Boolean expressions for the flip-flop inputs.

i.e. How do the inputs (say, J & K) to the flipflops depend on the current state and input

Step 2:

Use these expressions to find the actual flip-flop input values for each possible combination of present states and inputs.

i.e. Fill in the state table (with new intermediate columns)

Step 3:

Use flip-flop characteristic tables or equations to find the next states, based on the flip-flop input values and the present states.

Step 1: Flip-flop input equations

- For our example, the **flip-flop input equations** are:


$$J_1 = X' Q_0$$

$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$

$$K_0 = X'$$

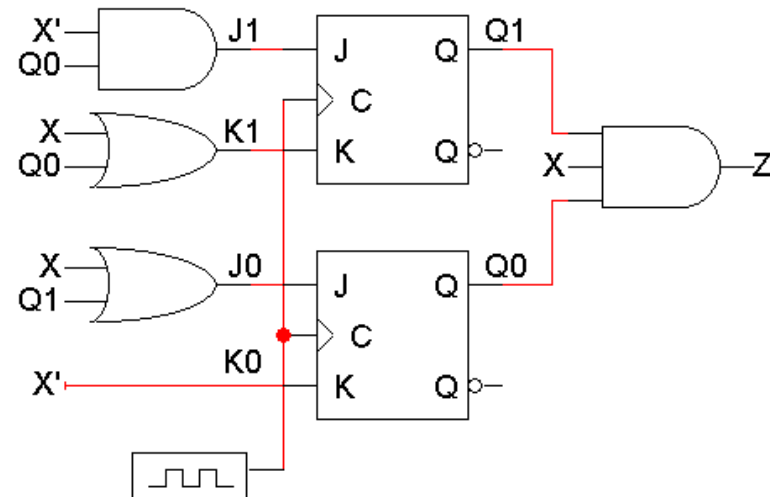- JK flip-flops each have *two* inputs, J and K. (D and T flip-flops have one input each.)



Step 2: Flip-flop input values

- With these equations, we can make a table showing J_1 , K_1 , J_0 and K_0 for the different combinations of present state Q_1Q_0 and input X .

$$J_1 = X' Q_0$$

$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$

$$K_0 = X'$$

Present State		Inputs X	Flip-flop Inputs			
Q_1	Q_0		J_1	K_1	J_0	K_0
0	0	0	0	0	0	1
0	0	1	0	1	1	0
0	1	0	1	1	0	1
0	1	1	0	1	1	0
1	0	0	0	0	1	1
1	0	1	0	1	1	0
1	1	0	1	1	1	1
1	1	1	0	1	1	0

Step 3: Find the next states

- Finally, use the JK flip-flop characteristic tables or equations to find the next state of *each* flip-flop, based on its present state and inputs.
- The general JK flip-flop characteristic equation is:

$$Q(t+1) = K'Q(t) + JQ'(t)$$

- In our example circuit, we have two JK flip-flops, so we have to apply this equation to *each* of them:

$$Q_1(t+1) = K_1'Q_1(t) + J_1Q_1'(t)$$

$$Q_0(t+1) = K_0'Q_0(t) + J_0Q_0'(t)$$

- We can also determine the next state for each input/current state combination directly from the characteristic table.

J	K	Q(t+1)	Operation
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

- Finally, here are the next states for Q_1 and Q_0 , using these equations:

$$Q_1(t+1) = K_1'Q_1(t) + J_1Q_1'(t)$$

$$Q_0(t+1) = K_0'Q_0(t) + J_0Q_0'(t)$$

Present State		Inputs X	FF Inputs				Next State	
Q_1	Q_0		J_1	K_1	J_0	K_0	Q_1	Q_0
0	0	0	0	0	0	1	0	0
0	0	1	0	1	1	0	0	1
0	1	0	1	1	0	1	1	0
0	1	1	0	1	1	0	0	1
1	0	0	0	0	1	1	1	1
1	0	1	0	1	1	0	0	1
1	1	0	1	1	1	1	0	0
1	1	1	0	1	1	0	0	1

The complete state table


- The table starts with **Present State** and **Inputs**.
 - Present State** and **Inputs** yield **FF Inputs**.
 - Present State** and **FF Inputs** yield **Next State**, based on the flip-flop characteristic tables.
 - Present State** and **Inputs** yield **Output**.

Present State		Inputs	FF Inputs				Next State		Outputs
Q_1	Q_0	X	J_1	K_1	J_0	K_0	Q_1	Q_0	Z
0	0	0	0	0	0	1	0	0	0
0	0	1	0	1	1	0	0	1	0
0	1	0	1	1	0	1	1	0	0
0	1	1	0	1	1	0	0	1	0
1	0	0	0	0	1	1	1	1	0
1	0	1	0	1	1	0	0	1	0
1	1	0	1	1	1	1	0	0	0
1	1	1	0	1	1	0	0	1	1

State Diagram


- We can also represent the state table graphically with a state diagram.
- A diagram corresponding to our example state table is shown below.

Present State		Inputs X	Next State		Outputs Z
Q ₁	Q ₀		Q ₁	Q ₀	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1

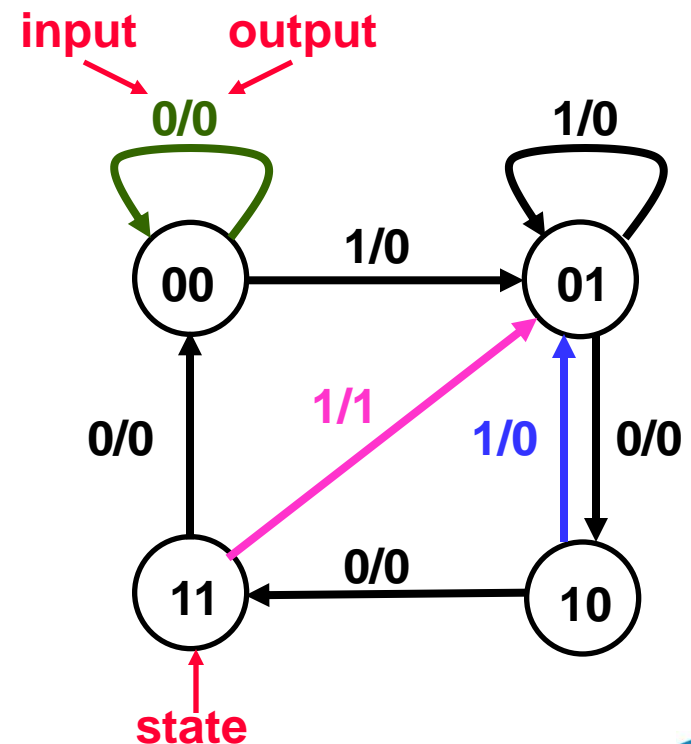

- Always check the size of your state diagrams.
 - If there are n flip-flops, there should be 2^n nodes in the diagram.
 - If there are m inputs, then each node will have 2^m outgoing arrows.
 - From each state
- In our example,
 - We have two flip-flops, and thus four states or nodes.
 - There is one input, so each node has two outgoing arrows.

Present State		Inputs X	Next State		Outputs Z
Q_1	Q_0		Q_1	Q_0	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1

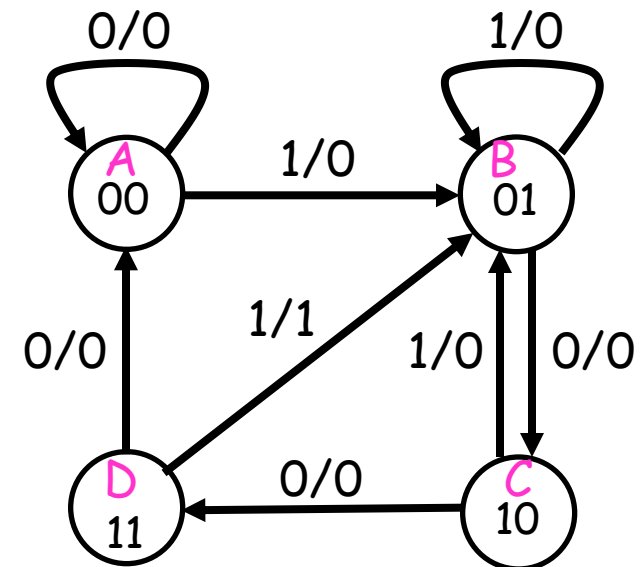

Sequential Circuit Analysis Summary

- To analyze sequential circuits, you have to:
 - Find Boolean expressions for the outputs of the circuit and the flip-flop inputs.
 - Use these expressions to fill in the output and flip-flop input columns in the state table.
 - Finally, use the characteristic equation or characteristic table of the flip-flop to fill in the next state columns.
- The result of sequential circuit analysis is a state table or a state diagram describing the circuit.